



BERZIET UNIVERSITY

Faculty of Engineering and Technology  
Electrical and Computer Engineering Department

**ANALOG ELECTRONICS**  
**ENEE2360**  
**PSpice project part1**

---

Student's name: Sara Issa

Student's ID: 1190673

Instructor's name: Dr. Naser Ismail

Section No. 2

Teacher assistant's name: Eng. Bilal Ismail

Date: 27.11.2021

# Abstract:

The aim of this project is to know how to use Pspice software to design and simulate a full wave center tap rectifier with filter, zener diode and transformer to change the voltage from Ac to Dc. Then, the comparison between the resulting values from the calculation process and the resulting values from the curves to find out the error percentage.

## Table of Contents:

1. Procedure and Discussion .....	3
1.1. Center tapped transformer .....	3
1.2. Center tapped full wave rectifier .....	3
1.1. The calculation before designing the circuit .....	4
1.2. The Circuit of Full wave Center Tab rectifier in Pspice .....	4
1.3. Plot $V_o(t)$ from circuit Simulation .....	5
1.4. Plot $V_c(t)$ from circuit Simulation .....	5
1.5. Plot $V_{ms1}(t)$ from circuit Simulation.....	5
1.6. Plot $V_{ms2}(t)$ from circuit Simulation.....	6
1.7. The calculation after designing the circuit .....	6
5. Conclusion .....	7
6. References .....	8

# 1. Procedure and Discussion:

To complete the design of the circuit shown in Figure NO.1, by using the given values in Table NO.1:

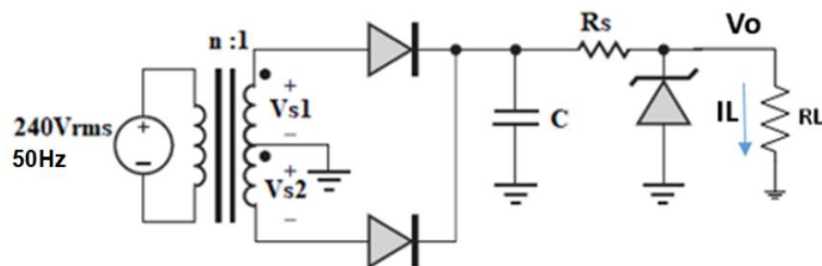


Figure NO.1: Circuit of Center Tapped Transformer Full-Wave Rectifier

Table NO.1 shows given values:

Load current	IL	0.14
Output voltage	Vo(avg)	20
Capacitor voltage	Vc(avg)	30
Pk-pk ripple at C	VLr,pp	4.8

**Center tapped transformer:** when an additional wire is connected across the exact middle of the secondary winding of a transformer, as shown in Figure NO.2:

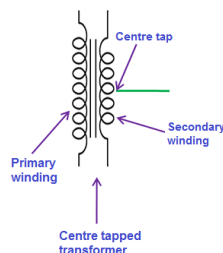


Figure NO.2: Center tapped transformer [1]

**Center tapped full wave rectifier:** is a type of rectifier which uses a center tapped transformer and two diodes to convert the complete AC signal into DC signal. It is made up of an AC source, a center tapped transformer, two diodes, and a load resistor, as shown in Figure NO.3:

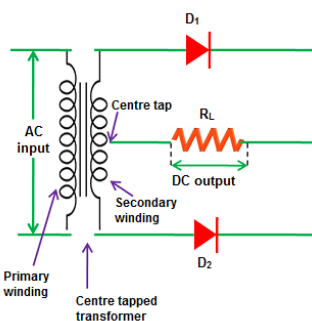


Figure NO.3: Center tapped full wave rectifier

### The calculation before designing the circuit (from the given values):

- From Datasheet for 1N4728A-1N4764A Zener diodes [2]:  
 $V_{ZT} = V_{o(avg)} = 20$  volt.  
 $I_{Z(max)} = 45\text{mA}$ .  
 $I_{ZT} = 12.5\text{mA}$ .
- By Ohm's Law:  $V_{o(avg)} = R_L I_L$ , then  $R_L = V_{o(avg)} / I_L = 20/0.14 = 142.857 \cong 143$  volt.
- In steady state:  $V_{mc} = V_{c(avg)} + (0.5 * V_{Lrp,p}) = 30 + (0.5 * 4.8) = 32.4$  volt.
- Simplified/Knee/Practical model: Diode ON replaced by 0.7 volt battery:  
 By KVL1:  $V_{ms1} = V_{mc} + 0.7 = 32.4 + 0.7 = 33.1$  volt.  
 By KVL2:  $V_{ms2} = V_{mc} - 0.7 = 32.4 - 0.7 = 31.7$  volt.
- $V_{mp} = V_{rms} * \sqrt{2} = 240 * \sqrt{2} = 339.4$  volt.
- By KCL:  $I_s = I_L + I_{Z(max)} = 0.14 + 45\text{mA} = 0.185 \text{ A} = 185 \text{ mA}$ .
- To find C:  
 $\Delta V = V_{Lrp,p} = V_{mc} / (2 * f_o * R * C) = I_s / (2 * f_o * C) \rightarrow 4.8 = 0.185 / (2 * 50 * C)$   
 Then  $C = 3.85416 * 10^{-4} = 385.4 \text{ uF}$ .
- $R_s = [V_{mc} - V_{o(avg)}] / I_s = (32.4 - 20) / 0.185 = 67.027 = 67 \text{ ohm}$ .
- In linear/ideal transformer:  $\frac{N_1}{N_2} = \frac{V_{mp}}{V_{ms1}} = \sqrt{\frac{L_1}{L_2}} = \frac{n}{1} = \frac{339.4}{33.1} = 10.25377644 \cong 10.25$   
 Assume  $L_2 = 1\text{mH}$ , then  $L_1 = 105.1399312 \text{ mH} \cong 105.14 \text{ mH}$ . And coupling = 1 "always in simulation".
- In linear/ideal transformer:  $\frac{N_1}{N_2} = \frac{V_{mp}}{V_{ms2}} = \sqrt{\frac{L_1}{L_2}} = \frac{n}{1} = \frac{339.4}{31.7} = 10.70662 \cong 10.71$   
 Assume  $L_2 = 1\text{mH}$ , then  $L_1 = 114.63181 \text{ mH} \cong 114.63 \text{ mH}$ . And coupling = 1 "always in simulation".

### The Circuit of Full wave Center Tab rectifier in Pspice:

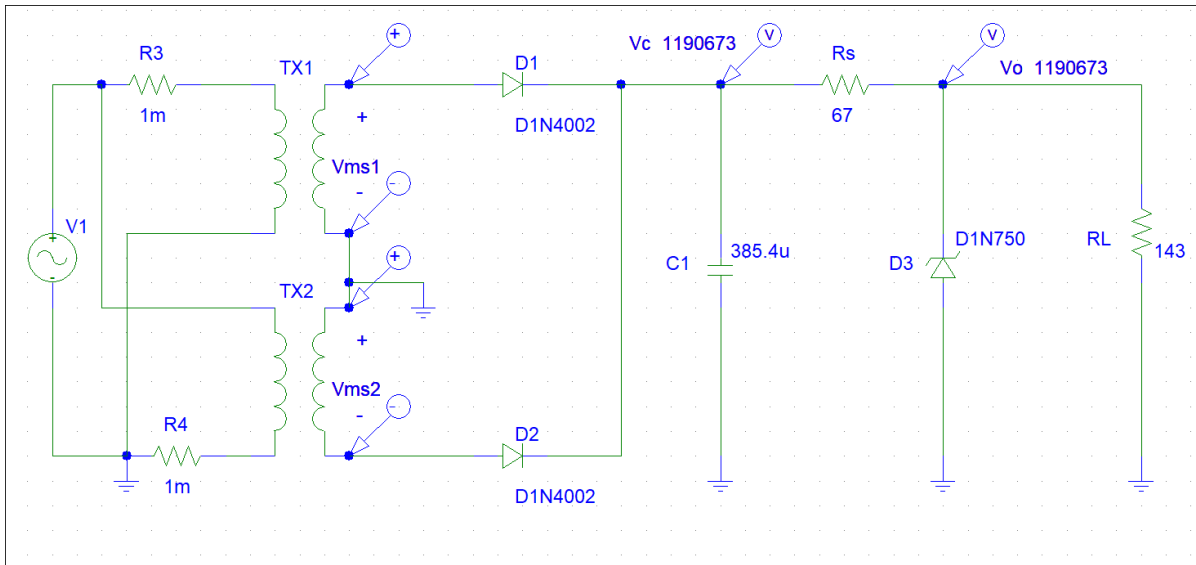


Figure NO.4: Circuit of Center Tapped Transformer Full-Wave Rectifier in Pspice

**Plot  $V_o(t)$  from circuit Simulation:**  $V_o$  curve in yellow,  $V_o = 20.006$  volt from the simulation and  $V_o = 20$  volt from given.

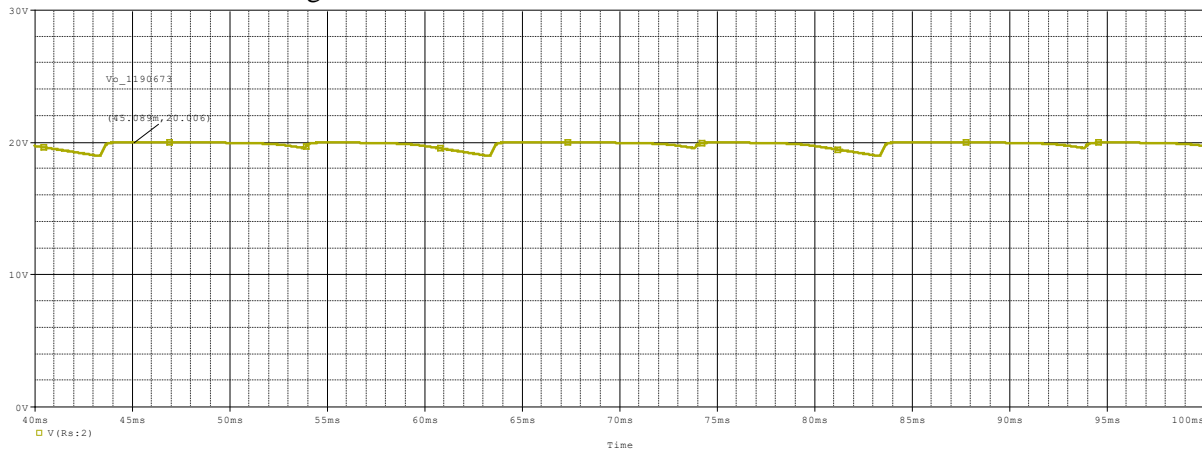


Figure NO.5:  $V_o(t)$  from circuit Simulation in Pspice

**Plot  $V_c(t)$  from circuit Simulation:**  $V_c$  curve in pink,  $V_c(\max) = 32.239$  volt and  $V_c(\min) = 27.83$  volt, then  $\Delta V = V_{Lrp,p} = V_{c(\max)} - V_{c(\min)} = 32.239 - 27.83 = 4.409$  volt from the simulation and  $\Delta V = V_{Lrp,p} = 4.8$  volt from given.

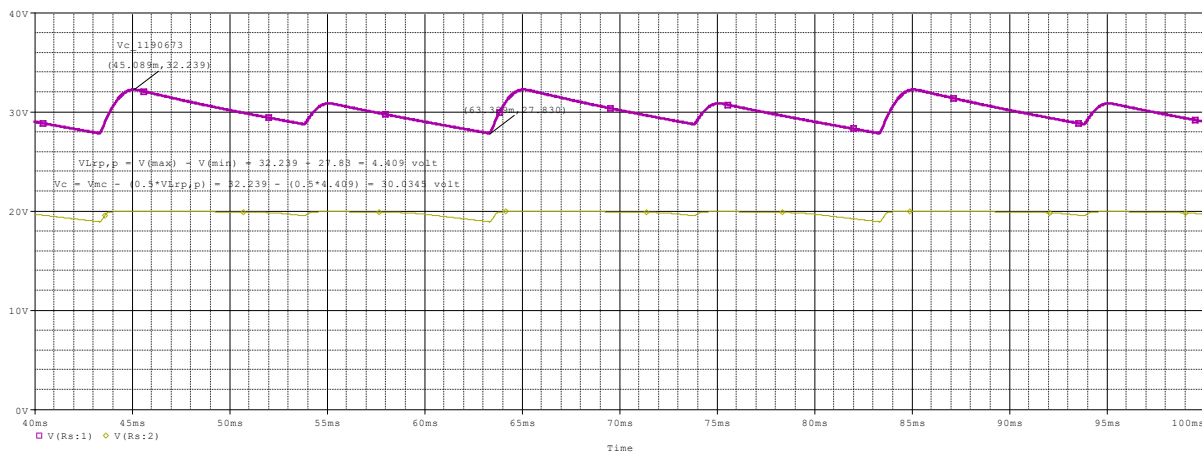


Figure NO.6:  $V_c(t)$  from circuit Simulation in Pspice

**Plot  $V_{ms1}(t)$  from circuit Simulation:**  $V_{ms1}$  curve in green,  $V_{ms1} = 33.099$  volt from the simulation and  $V_{ms1} = 33.1$  volt from the calculation.

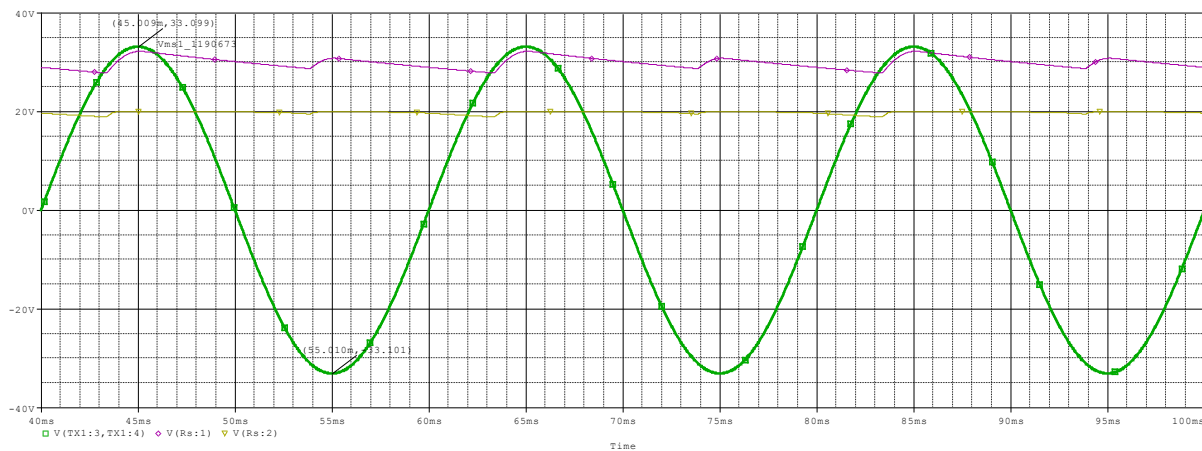


Figure NO.7:  $V_{ms1}(t)$  from circuit Simulation in Pspice

**Plot Vms2(t) from circuit Simulation:** Vms2 curve in blue, Vms2 = 31.699 volt from the simulation and Vms2 = 31.7 volt from the calculation.

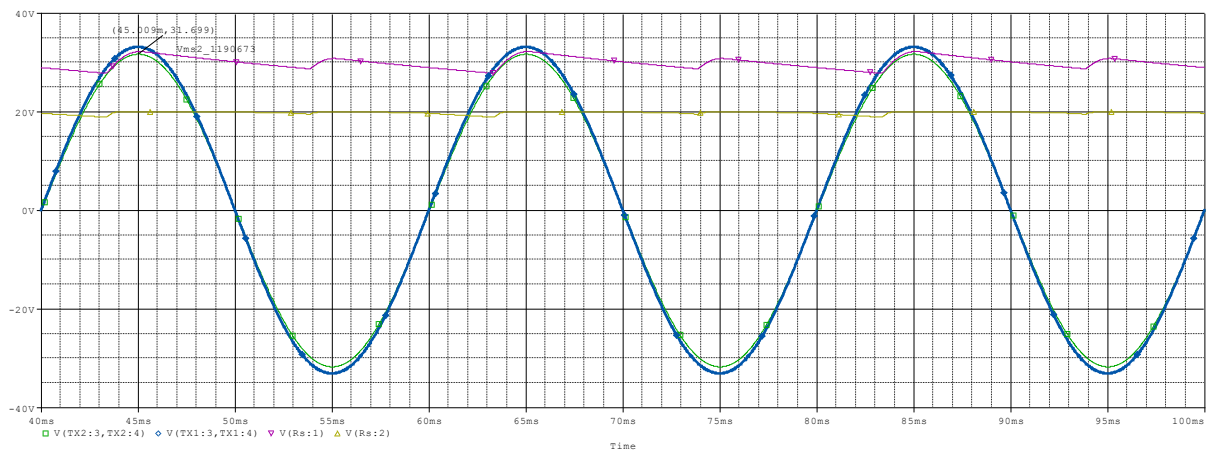


Figure NO.6: Vms2(t) from circuit Simulation in Pspice

**The calculation after designing the circuit (from the curve):**

- From first curve:  $V_o = 20.006$  volt.
- From second curve:  $V(\max) = 20.32.239$  volt and  $V(\min) = 27.83$ , then  $\Delta V = V_{Lrp,p} = V_{c(\max)} - V_{c(\min)} = 32.239 - 27.830 = 4.409$  volt.
- From third curve:  $V_{ms1} = 33.099$  volt.
- From fourth curve:  $V_{ms2} = 31.699$  volt.
- $V_{mc} = V(\max) = V_c + (0.5 * V_{Lrp,p})$ , then  $V_c = V_{mc} - (0.5 * V_{Lrp,p}) = 32.239 - (0.5 * 4.409) = 30.0345$  volt  $\cong 30$  volt.

## 2. Conclusion:

Comparison of the results between simulated values of  $V_o(t)$ ,  $V_c(t)$ , and the ripple voltage to hand calculations, as shown in Table NO.1:

Name of voltage	simulated values	Hand calculations values
$V_o(t)$	20.006 volt	20 volt
$V_c(t)$	30.0345 volt	30 volt
Ripple voltage $V_{L_{rpp}}$	4.409 volt	4.8 volt
$V_{ms1}(t)$	33.099 volt	33.1 volt
$V_{ms2}(t)$	31.699 volt	31.7 volt

From the previous table, it was found that the values of  $V_o(t)$ ,  $V_c(t)$ ,  $V_{ms1}(t)$  and  $V_{ms2}(t)$  were very similar, while the value of the ripple voltage differed by a very small amount. It could be that the value of  $C$  was not calculated correctly 100% because we considered that the current passing through the zener diode =  $I_z(\max)$ , then the value of  $V_c$  was not accurate 100%.

Error percentage in Full wave Center Tab rectifier:

Error percentage =  $[V_c(\text{simulation}) - V_c(\text{given})] / V_c(\text{given}) * 100\% = (30.0345 - 30) / 30 * 100\% = 0.115$  very small percentage, so it's accepted.



### 3. References:

1. " Full wave rectifier," 24 NOV 2021. [Online]. Available: <https://www.physics-and-radio-electronics.com/electronic-devices-and-circuits/rectifier/fullwaverectifier.html>.
2. "1N4747A Datasheet," 22 NOV 2021. [Online]. Available: <https://pdf1.alldatasheet.com/datasheet-pdf/view/972142/ZSELEC/1N4747A.html>.
3. "lecture notes," 20 NOV 2021. [Online]. Available: [https://drive.google.com/drive/folders/1BM0tKtk\\_tsWvnqLaALTTrSv28DYf2cHz](https://drive.google.com/drive/folders/1BM0tKtk_tsWvnqLaALTTrSv28DYf2cHz).